

Real Time Imaging

State Machine on NEXYS 4

IOANNIS TSAGKATAKIS
KARIM BOTROS



State Machine Encoding

```
architecture sm_decoder_impl of sm_decoder is
```

```
-- STATE ENCODINGS
```

```
constant STATE1 : std_logic_vector(4 downto 0) := "001" & "00";
```

```
constant STATE2 : std_logic_vector(4 downto 0) := "010" & "00";
```

```
constant STATE3 : std_logic_vector(4 downto 0) := "011" & "01";
```

```
constant STATE4 : std_logic_vector(4 downto 0) := "100" & "11";
```

```
constant STATE5 : std_logic_vector(4 downto 0) := "101" & "00";
```

```
signal CUR_STATE : std_logic_vector(4 downto 0);
```

```
begin
```

```
-- Hard wires
```

```
S1 <= CUR_STATE(0);
```


```
S2 <= CUR_STATE(1);
```


```
ISTATE <= CUR_STATE(4 downto 2);
```

ISTATE

S2 S1


sm_decoder

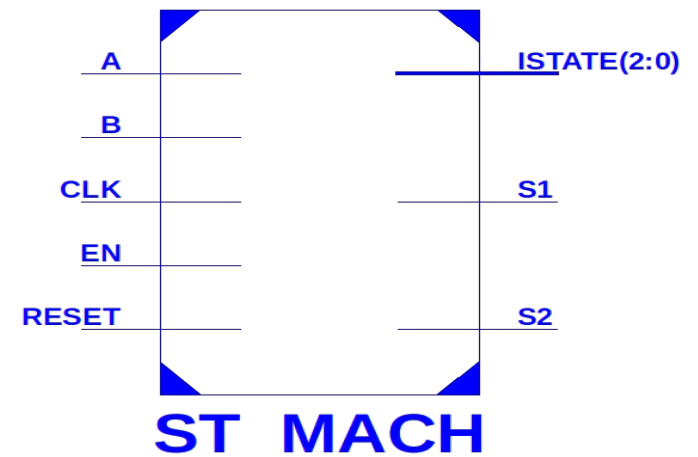

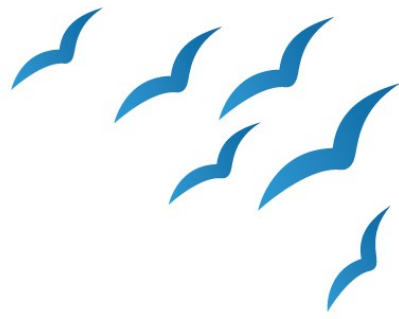



Operation

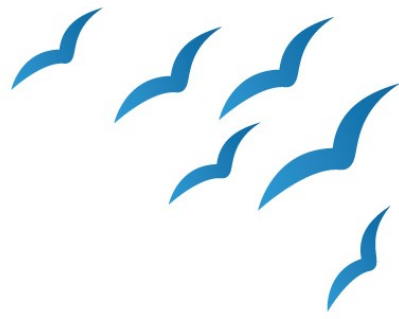- Input
 - Switch A
 - Switch B
 - RESET
 - ENABLE Btn
- Output
 - S1 & S2
 - 2 right leds
 - 3color led
 - Internal State
 - 5 left leds
 - 7 Segment disp.





The Output Leds Driver

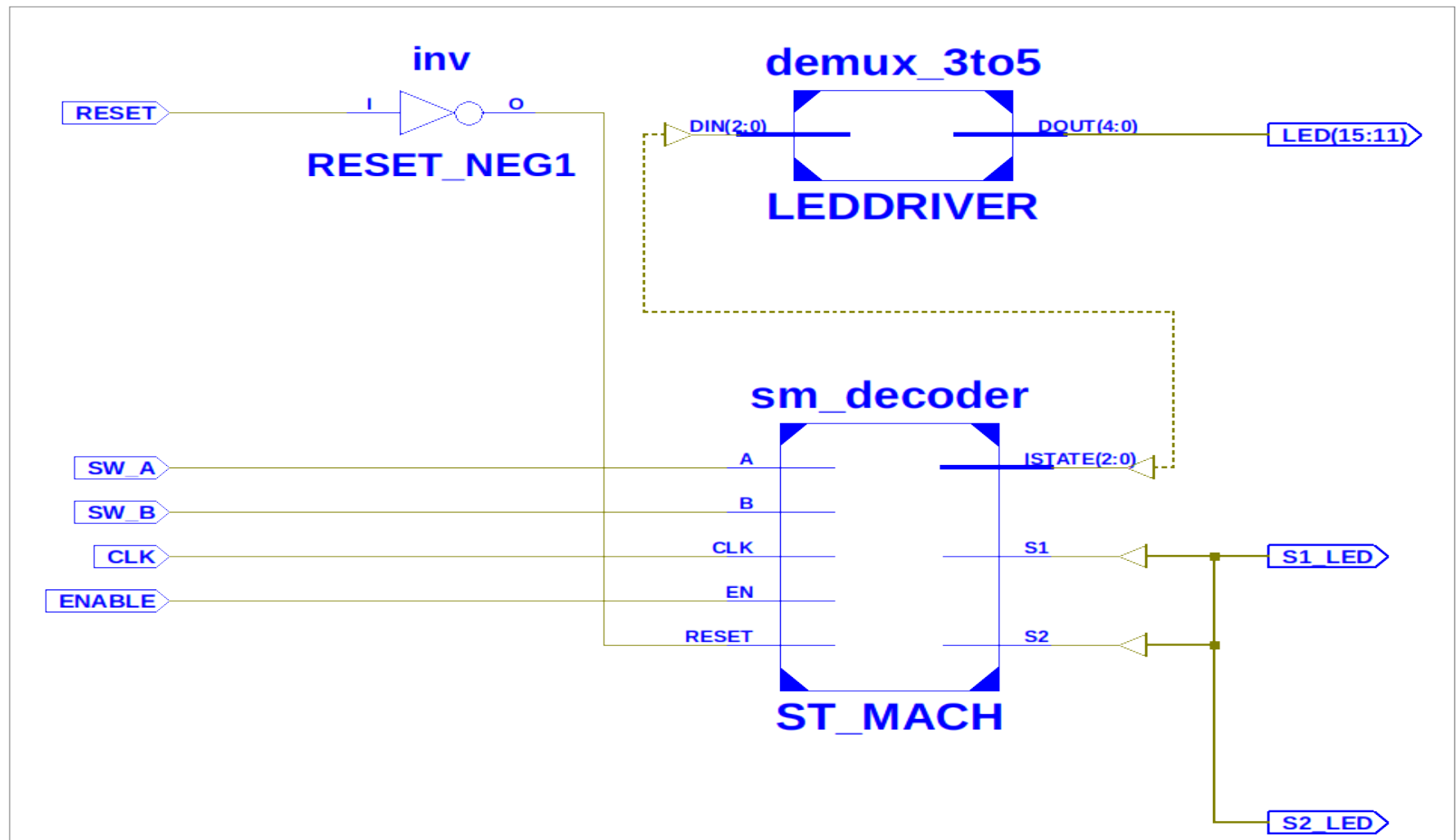

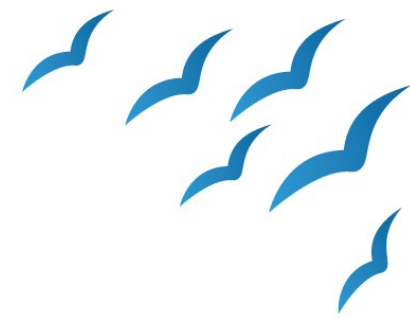



The RGB Led Driver

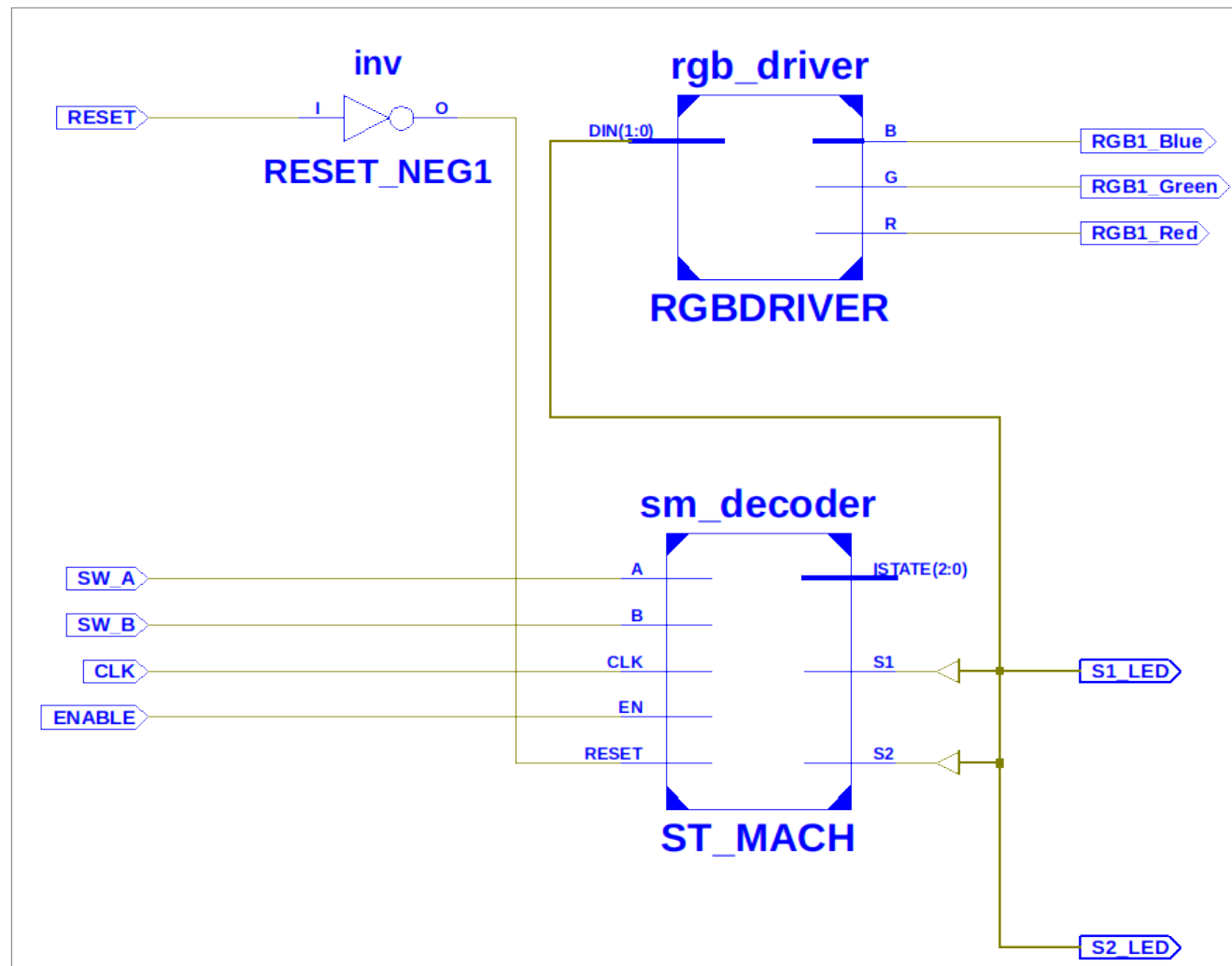

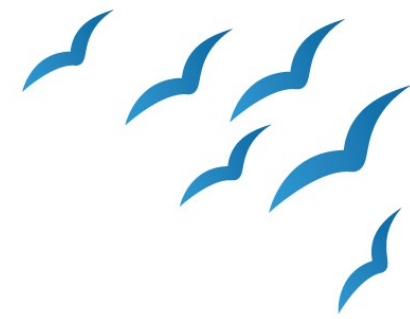

The & Segment Driver

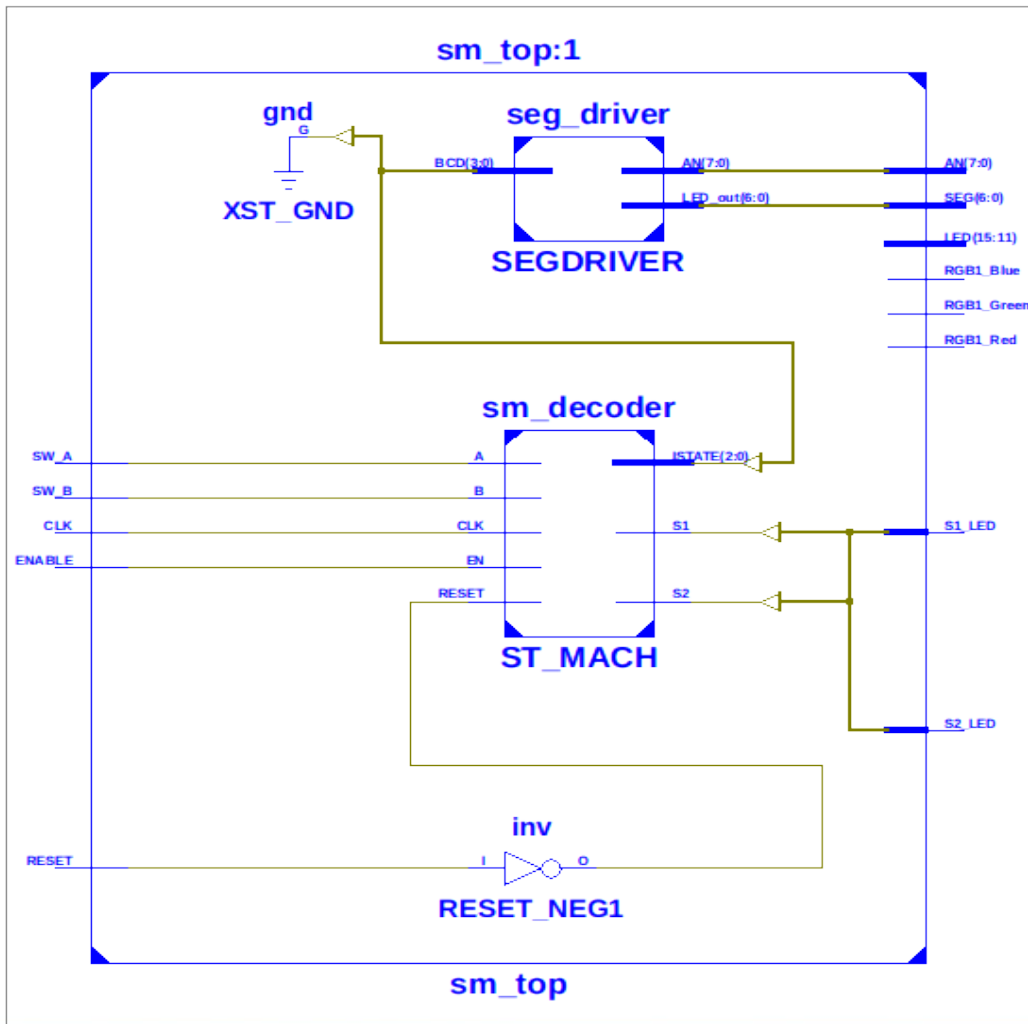

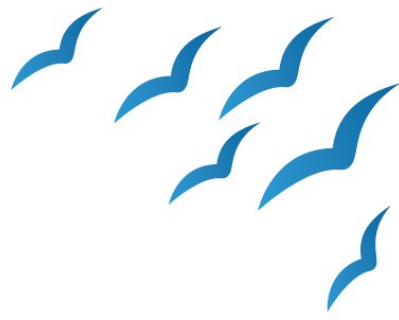

Demo Time

Code on Github

https://github.com/jtsagata/nexys4_sm_lab